



FUTURE KIT

HIGH QUALITY ELECTRONIC KITS

วงจรขยายเสียงพูดขนาดเล็ก 2 วัตต์
MINI MEGAPHONE
CODE 672

ข้อมูลทางด้านเทคนิค
- ใช้แหล่งจ่ายไฟขนาด 4.5-12 โวลท์ดีชี
- กินกระแสสูงสุดประมาณ 300 มิลลิแอมป์ ที่ 12 โวลท์
- กำลังขยายสูงสุด 2 วัตต์ (ที่ลำโพง 8 Ω ห้อง 2 วัตต์, 12 โวลท์ กินกระแสสูงสุดประมาณ 1.5 แอมป์)

- มีวอลุ่มลดลงความดังของเสียง
- อัตราส่วน S/N : 80 ดีบี
- ตอบสนองความถี่ตั้งแต่ 20Hz-20 kHz ที่ -3 ดีบี
- ขนาดแผ่นวงจรพิมพ์ : 2.34 x 1.42 นิ้ว

การทำงานของวงจร

การทำงานจะเริ่มจากเมื่อสัญญาณเสียงเข้ามาที่ไมค์ สัญญาณเสียงที่เข้ามาจะถูกแปลงเป็นสัญญาณไฟฟ้า แล้วจะถูกส่งไปเข้า TR1 โดยผ่าน C11 ซึ่ง TR1 นี้จะทำการขยายสัญญาณให้มีความแรงขึ้น จากนั้นสัญญาณที่ถูกขยายแล้วจะออกไปทางขา C ของ TR1 ผ่าน VR1 ซึ่งทำหน้าที่ปรับความเหมาะสมของสัญญาณที่จะถูกนำไปขยายอีกรอบหนึ่ง โดยสัญญาณที่ได้จะไปเข้าขา 3 ของ IC1 IC1 นี้จะทำหน้าที่เป็นวงจรขยายเสียงขนาด 2 วัตต์ โดยจะทำการขยายความแรงของสัญญาณให้มากขึ้นไปอีก ก่อนจะถูกส่งออกไปเข้าลำโพงเพื่อเปล่งเป็นสัญญาณเสียงต่อไป

การประกอบวงจร

รูปการลงอุปกรณ์และการต่ออุปกรณ์ภายในรูปที่ 2 ในการประกอบวงจรจะเริ่มจากอุปกรณ์ที่มีความสูงที่สุดก่อน เพื่อความสวยงามและการประกอบที่ง่าย โดยให้เริ่มจากไดโอดตามด้วยตัวต้านทานและไอล์วัตต์ไปเรื่อยๆ สำหรับอุปกรณ์ที่มีชั้นต่างๆ เช่น ไดโอด, คานเชลล์เซตเตอร์, แบตเตอรี่, ทรานซิสเตอร์ เป็นต้น ควรใช้ความระมัดระวังในการประกอบวงจรก่อนการใส่อุปกรณ์เหล่านี้ จะดีกว่าที่เข้าไปในวงจรที่อุปกรณ์ที่ติดต่ออยู่ เพราะอาจทำให้อุปกรณ์ที่ร่องรอยเสียหายได้ วิธีการดูขั้วและการใส่อุปกรณ์นั้นได้แสดงไว้ในรูปที่ 3 และ ในการบัดกรีให้ขั้วแรงงานดีไม่เกิน 40 วัตต์ และใช้ตะเก็บบัดกรีที่มีอัตราส่วนของคีบกัดและตะเก็บอยู่ระหว่าง 60/40 รวมทั้งจะต้องมีน้ำยาประสานอยู่ภายในตะเก็บด้วย หลังจากที่ได้ใส่อุปกรณ์และบัดกรีเรียบร้อยแล้ว ให้ทำการตรวจสอบความถูกต้องอีกรอบหนึ่ง เพื่อให้เกิดความมั่นใจแก่ตัวเราเอง แต่ถ้าเกิดใส่อุปกรณ์ผิดตำแหน่ง ควรใช้ที่อุดดูดที่ว่างหรือลวดซับตะกั่ว เพื่อป้องกันความเสียหายที่อาจจะเกิดกับสายวงจรพิมพ์ได้

การทดสอบ

ก่อนทำการต่อแหล่งจ่ายไฟเข้าวงจร ให้ทำการหมุนวอลุ่มไปทางซ้ายมือสุด จากนั้นนำแหล่งจ่ายไฟขนาด 4.5-12 โวลท์ดีชีต่อเข้าวงจร ค่อยๆ หมุนวอลุ่มพร้อมกับทดลองทุกดีไซน์ที่ได้ยินเสียงของมาทางลำโพง ส่วนความดังของเสียงนั้นจะขึ้นอยู่กับการปรับวอลุ่มของเรารา

ขยายเสียงพูดขนาดเล็ก 2 วัตต์

MINI MEGAPHONE

CODE 672

LEVEL 1

This economical amplifier/speaker combination is an ideal class room project. The FK672 is also supplied with a dynamic microphone and its circuit incorporates a preamplifier with a volume control.

Technical data

- Power supply : 4.5-12VDC.
- Electric current consumption : 300mA (max.) @ 12VDC.
- Output power : 2W.max. (using a loudspeaker 8Ω 2W/power supply 12V/1.5A. max.)
- Adjustable level sound by potentiometer.
- S/N ratio : 80dB (A weighted)
- Frequency response : 20Hz to 20kHz (-3dB)
- IC board dimension : 2.34 in x 1.42 in

How does to work

When have sound signal to MIC, this signal is changed from audio signal to AC signal. AC signal will amplify by TR1 preamplifier through C11. The resulting AC signal is coupled to the volume control VR1 by C1, which also blocks any DC voltage that may be present on the signal. VR1 is used to adjust the input signal to amplifier IC1. This amplifier can supply 2W into the 8Ω loudspeaker with a supply voltage of 12V. After amplifier, this AC signal will be changed to audio signal by loudspeaker.


Circuit Assembly

The assembly of components is shown in Fig. 2. For good looking and easy assembly, the shorter components should be first installed - starting with low resistant components and then the higher. An important thing is that diodes, electrolytic capacitors, and transistors shall be carefully assembled before mounting them onto their right anode/cathode of the IC board otherwise it might cause damage to the components or the circuit. Configuration of the anode and the cathode is shown in Fig 3. Use the soldering iron/gun not exceeding 40 watts and the solder of tin-lead 60:40 with flux within. Recheck the correctness of installation after soldering. In case of wrong position, just use lead absorber or lead extractor wire to avoid probable damage to the IC.


Testing

Before apply the power supply to the circuit, adjust volume control VR1 max. counterclockwise. And then apply the power supply 4.5 to 12 VDC to circuit. Speak into MIC and adjust VR1 clockwise slowly, you will hear your sound from a loudspeaker.

Figure 1. The Mini Megaphone Circuit

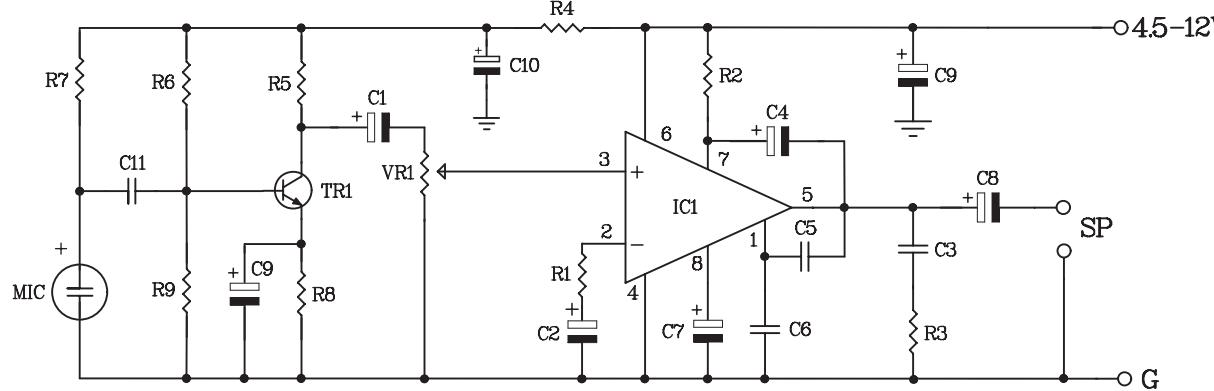

FK672

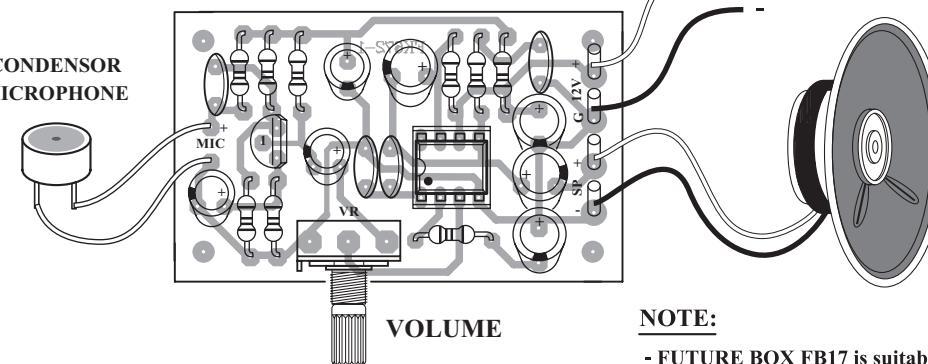

SPEAKER
8 Ω 0.25W

NOTE:

- FUTURE BOX FB17 is suitable for this kit.
- If you want to using amplifier 2W max., you must changed the value of loudspeaker to 8 Ω 2W and power supply to 12V. 1.5A. max.
- In case of there is the feedback sound ("vee" sound) form speaker, to take off the capacitor C9.

Figure 2. Circuit Assembling

NO.1

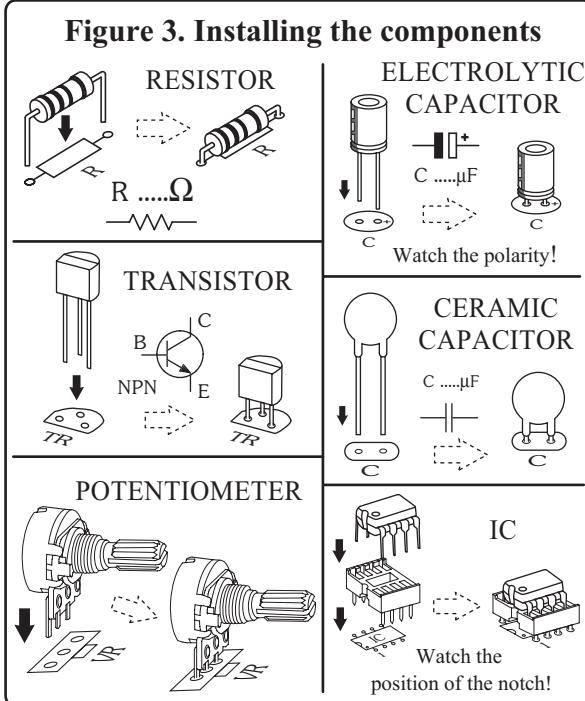


Figure 3. Installing the components